

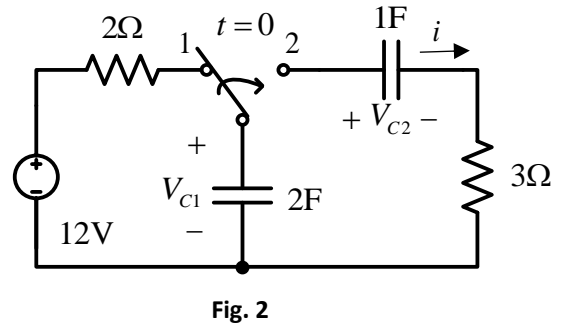
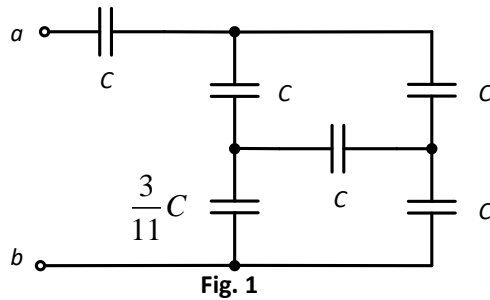



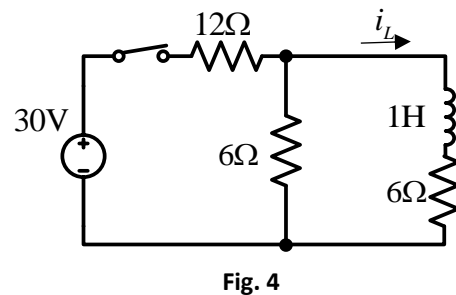
- Find the equivalent capacitance between terminals a and b in the circuit **Fig. 1**.
- In **Fig. 2** the switch has been placed at position 1 for a long time before moving to position 2 at $t=0$. If $V_{C2}(0^-) = 0$, (a) find $i(t)$ for $t>0$; (b) find the energy dissipated by the $3\text{-}\Omega$ resistor.



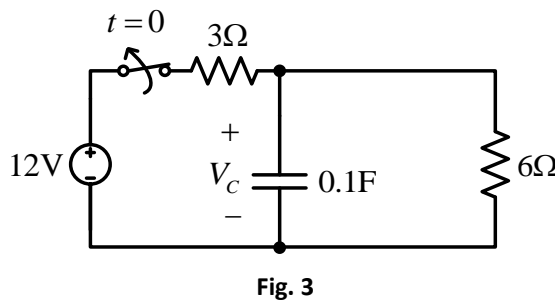- Find $v_C(t)$ for $t>0$ in the circuit **Fig. 3** if the switch opens at $t=0$.
- In the circuit of **Fig. 4**, the switch closes at $t=0$. If the initial value of i_L is zero, find $i_L(t)$ for $t>0$.



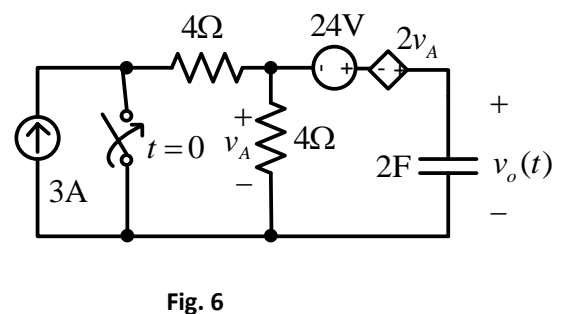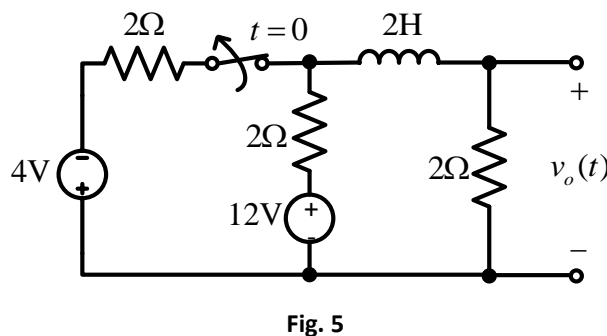- The switch in **Fig. 5** has been closed for a long time before opening at $t=0$. Find the voltage $v_o(t)$ for $t>0$.
- The switch in **Fig. 6** has reached steady-state before the switch closes at $t=0$, find the voltage $v_o(t)$ for $t>0$.




電路學(一) 第三次考試 參考解答

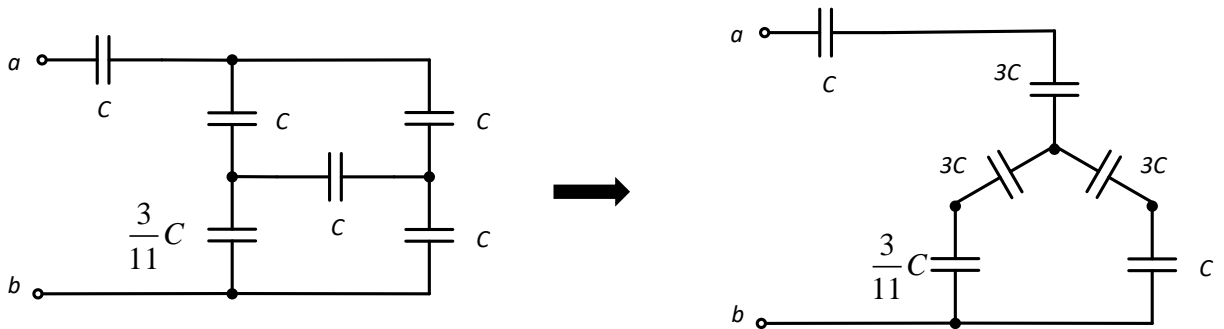1. 將圖 1 利用 Δ -Y 轉換, 如下圖所示

$$C_1^{-1} = \frac{\frac{1}{C} \times \frac{1}{C}}{\frac{1}{C} + \frac{1}{C} + \frac{1}{C}} = \frac{1}{3C}, \quad C_1 = 3C = C_2 = C_3$$

$$C_{ab} = C // 3C // \left[(3C // \frac{3}{11}C) + (3C // C) \right] = C // 3C // C = \frac{3}{7}C (\text{F})$$



2. (a) 電流初值: $i(0) = \frac{12}{3} = 4\text{A}$, 電流終值: $i(\infty) = 0\text{A}$

$$\text{令 } i(t) = A + Be^{-\frac{t}{\tau}}, \quad i(0) = A + B = 4, \quad i(\infty) = A = 0, \quad B = 4$$

$$\tau = RC = 3 \cdot \frac{2}{2+1} = 2\text{s}, \quad \text{最後得知 } i(t) = 4e^{-\frac{t}{2}}\text{A}$$

(b) 計算開關閉合前後的儲能差值

$$Q = CV = 2 \cdot 12 = 24\text{F},$$


$$t = \infty, \quad C_1 \cdot V_{c1} + C_2 \cdot V_{c2} = 3V_f = 24, \quad V_f = 8\text{V}, \quad V_{c1} = V_{c2}$$

$$\text{開關閉合前, } t = 0, \quad W_0 = \frac{1}{2} \cdot C_1 \cdot V_1^2 = \frac{1}{2} \cdot 2 \cdot 12^2 = 144\text{J}$$


$$\text{開關閉合後, } t = \infty, \quad W_1 = \frac{1}{2} \cdot C_1 \cdot V_f^2 + \frac{1}{2} \cdot C_2 \cdot V_f^2 = \frac{1}{2} \cdot 2 \cdot 8^2 + \frac{1}{2} \cdot 1 \cdot 8^2 = 96\text{J}$$

$$\Delta W = W_1 - W_2 = 144 - 96 = 48\text{J}$$

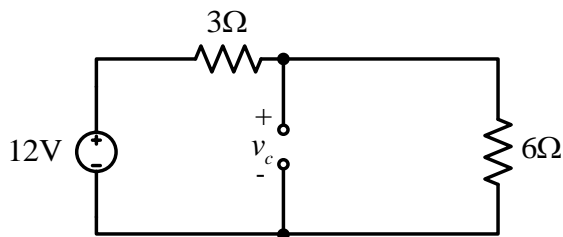3. 開關閉合時,電壓初值: $v_c(0) = 12 \cdot \frac{6}{3+6} = 8V$





$t = 0$ 時,開關打開,電壓終值: $v_c(\infty) = 0V$

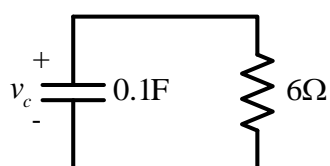

$$v_c(t) = A + Be^{-\frac{t}{\tau}}, \quad v_c(0) = A + B = 8, \quad v_c(\infty) = A = 0, \quad \tau = RC = 6 \cdot 0.1 = 0.6s$$

最後得知 $v_c(t) = 8e^{-\frac{t}{0.6}}V$

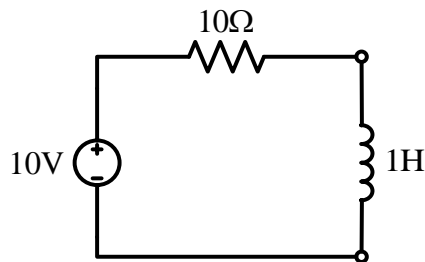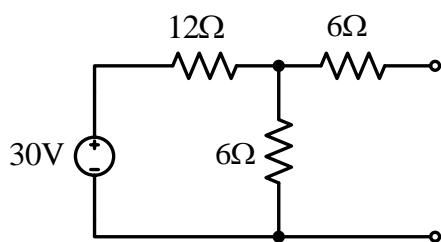4. 電流初值: $i_L(0) = 0A$; $t = 0$ 時開關閉合,由電感看入求戴維寧等效電路



$$R_{th} = (12 // 6) + 6 = 10\Omega, \quad V_{th} = 30 \cdot \frac{6}{12+6} = 10V$$

$$i_L(\infty) = \frac{10}{10} = 1A, \quad i_L(t) = A + Be^{-\frac{t}{\tau}}, \quad i_L(0) = A + B = 0$$

$$i_L(\infty) = A = 1, \quad B = -1, \quad \tau = \frac{L}{R} = \frac{1}{10} = 0.1s$$


最後得知 $i_L(t) = 1 - e^{-\frac{t}{0.1}} = 1 - e^{-10t}A$

5. 將圖五 a 點電壓設為 V_a

$$\frac{V_a + 4}{2} + \frac{V_a - 12}{2} + \frac{V_a}{2} = 0$$

$$V_a + 4 + V_a - 12 + V_a = 0$$

$$V_a = \frac{8}{3} \text{ V}$$

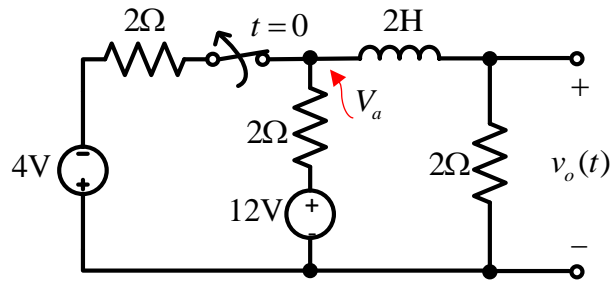


$$i(0) = \frac{8}{2} = \frac{4}{3} \text{ A} , \quad i(\infty) = \frac{12}{2+2} = 3 \text{ A} ,$$

$$i(t) = A + B e^{-\frac{t}{\tau}} , \quad i(0) = A + B = \frac{4}{3} , \quad i(\infty) = A = 3 , \quad B = -\frac{5}{3} ,$$

$$\tau = \frac{L}{R} = \frac{2}{4} = 0.5 \text{ s} , \quad i(t) = 3 - \frac{5}{3} e^{-\frac{t}{0.5}} = 3 - \frac{5}{3} e^{-2t} \text{ A}$$

$$\text{最後得知 } v_o(t) = 2 \cdot i(t) = 6 - \frac{10}{3} e^{-2t} \text{ V}$$

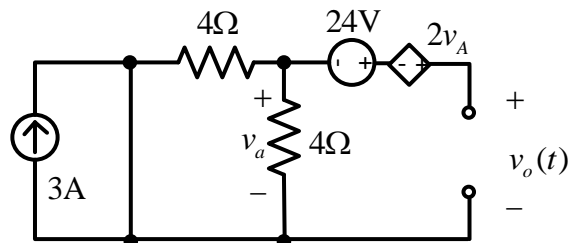6. 開關閉合前, $v_A = 3 \cdot 4 = 12 \text{ V}$, $v_o(0) = v_A + 24 + 2v_A = 60 \text{ V}$



開關閉合後, 由 $v_o(t)$ 看入求戴維寧等效電路, 此時 4Ω 無電流通過, $v_A = 0 \text{ V}$, 因此開路電壓 $V_{oc} = 24 \text{ V}$; 利用克希荷夫電路定律寫出下列方程式 $24 = v_A + 2v_A$, $v_A = 8 \text{ V}$,


得到開路電流 $I_{sc} = \frac{v_A}{4} \cdot 2 = \frac{8}{4} \cdot 2 = 4 \text{ A}$, 因此求得 $R_{th} = \frac{V_{oc}}{I_{sc}} = 6\Omega$ 。

$$v_o(\infty) = 24 \text{ V}$$

$$v_o(t) = A + B e^{-\frac{t}{\tau}} , \quad v_o(0) = A + B = 60$$

$$v_o(\infty) = A = 24 , \quad B = 36$$

$$\tau = RC = 6 \cdot 2 = 12 \text{ s}$$

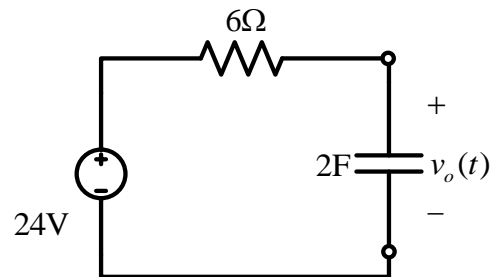

$$\text{最後得知 } v_o(t) = 24 + 36 e^{-\frac{t}{12}} \text{ V}$$