

每題 20 分，滿分 120 分。可使用計算器，不得參考任何書本及筆記。

- Find the mesh currents I_1 and I_2 in the circuit shown in **Fig. 1**.
- If an $8\text{-}\Omega$ load is connected to terminals a, b of the network shown in **Fig. 2**, $V_{ab}=16\text{ V}$. If a $2\text{-}\Omega$ load is connected to the terminals, $V_{ab}=8\text{ V}$. Find V_{ab} if a $20\text{-}\Omega$ load is connected to the terminals. (Hint: Assume a Thévenin equivalent circuit in the black box.)

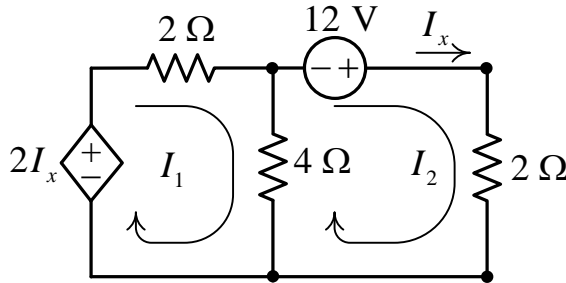


Fig. 1

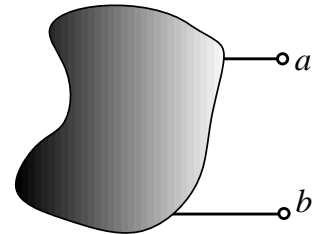


Fig. 2

- In the circuit shown in **Fig. 3**, $v_1=1.2\text{ V}$, $v_2=3.4\text{ V}$. Find the output voltage v_o and the current i .
- In the circuit shown in **Fig. 4**, $v_1=0.5\text{ V}$, $v_2=1.0\text{ V}$, $v_3=1.5\text{ V}$. Find the output voltage v_o .

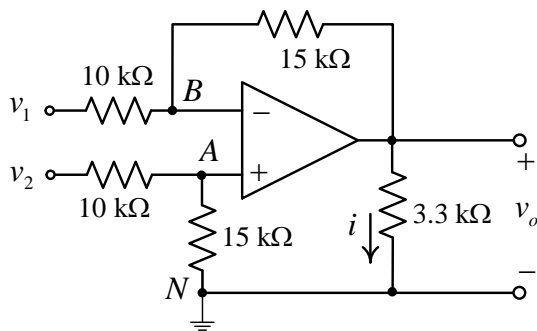


Fig. 3

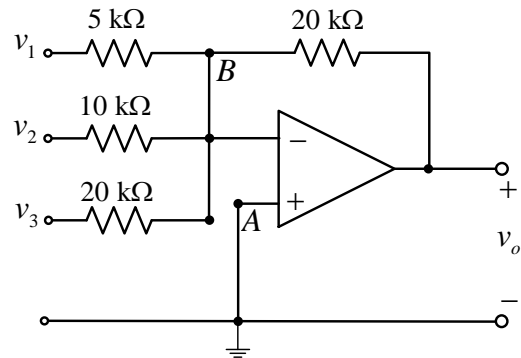


Fig. 4

- Find the Thévenin equivalent circuit (V_{th} and R_{th}) at the terminals a and b of the circuit of **Fig. 5**.
- In the circuit of **Fig. 6**, find the Thévenin equivalent circuit seen by resistor R_L , and determine the maximum power that can be transferred to R_L .

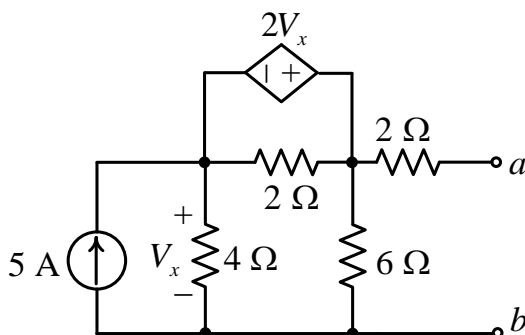


Fig. 5

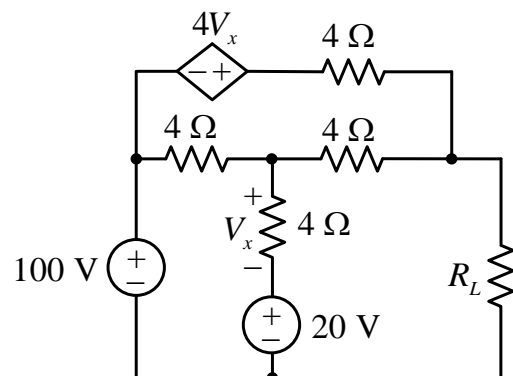


Fig. 6

每題 20 分，滿分 120 分。可使用計算器，不得參考任何書本及筆記。

- Find the mesh currents I_1 and I_2 in the circuit shown in Fig. 1.
- If an $8\text{-}\Omega$ load is connected to terminals a, b of the network shown in Fig. 2, $V_{ab} = 16\text{V}$. If an $2\text{-}\Omega$ load is connected to terminals, $V_{ab} = 8\text{V}$. Find V_{ab} if a $20\text{-}\Omega$ load is connected to the terminals.
(Hint: Assume Thévenin equivalent circuit in the black box.)

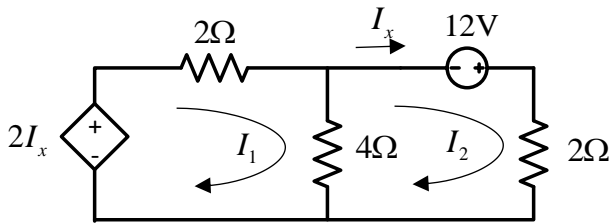


Fig. 1

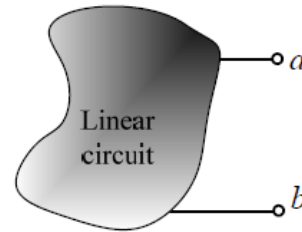


Fig. 2

- In the circuit shown in Fig. 3, $v_1 = 1.2\text{V}$, $v_2 = 3.4\text{V}$. Find the output voltage v_o and the current i .
- In the circuit shown in Fig. 4, $v_1 = 0.5\text{V}$, $v_2 = 1.0\text{V}$, $v_3 = 1.5\text{V}$. Find the output voltage v_o .

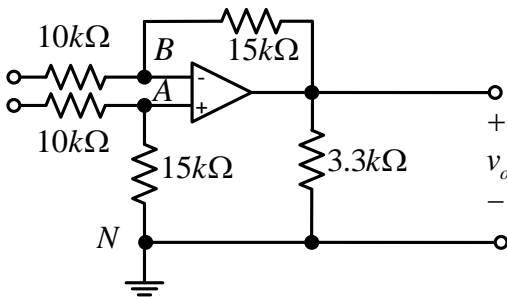


Fig. 3

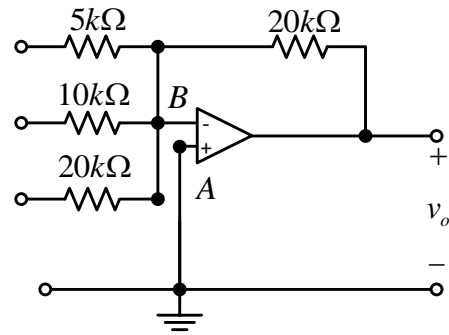


Fig. 4

- Find the Thévenin equivalent circuit (V_{th} and R_{th}) at the terminals a and b of the circuit of Fig. 5.
- In the circuit of Fig. 6, find the Thévenin equivalent circuit seen by resistor R_L , and determine the maximum power that can be transferred to R_L .

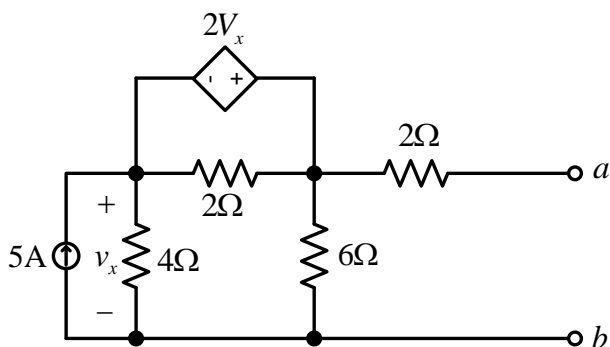


Fig. 5

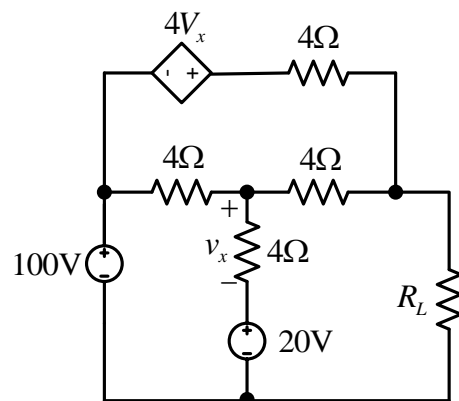


Fig. 6



電路學(一) 第二次考試 參考解答

1. 在所求出之網路的迴路中, 利用克希荷夫電壓定律寫出兩迴路方程式以求出各迴路之電流

$$\begin{cases} 2I_x = 2I_1 + 4(I_1 - I_2) \\ 12 = 2I_2 + 4(I_2 - I_1) \\ I_2 = I_x \end{cases}$$


求得 $I_1 = 6A, I_2 = 6A$

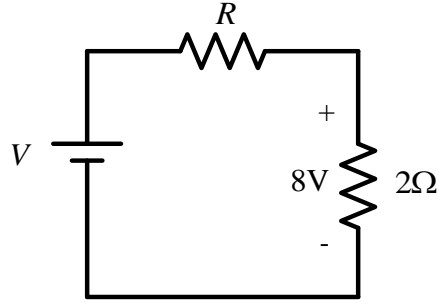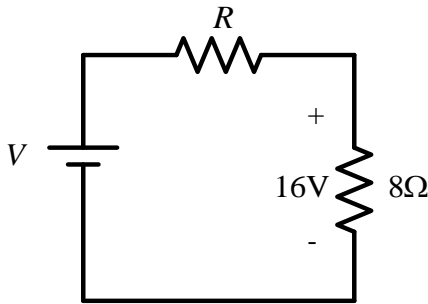2. 假設電壓源裡有一內阻: R 及電壓: V , 依照題目敘述可以列出兩個方程式, 求得內阻: R 及電壓: V 。



$$\begin{cases} V \times \frac{8}{R+8} = 16 \\ V \times \frac{2}{R+2} = 8 \end{cases}$$

求解得知 $V = 24V, R = 4\Omega$

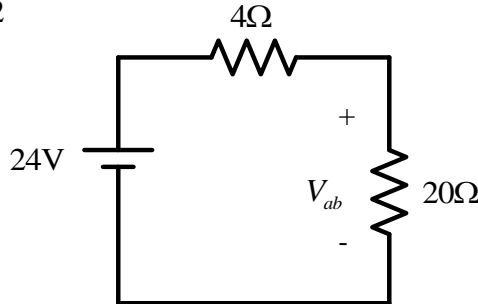

當 V_{ab} 是 20Ω 時,

$$V_{ab} = 24 \times \frac{20}{4+20} = 20V$$

3. 利用克希荷夫電流定律求出 V_o 和 i

$$V_A = 3.4 \times \frac{15k}{10k+15k} = 2.04V = V_B$$


$$\frac{2.04-1.2}{10k} - \frac{V_o-2.04}{15k} = 0$$

$$V_o = 3.3V, i = \frac{3.3}{3.3k} = 1mA$$


4. 圖 4 是一個反向放大器, 可用公式求得 V_o

$$V_o = -(0.5 \times \frac{20k}{5k} + 1 \times \frac{20k}{10k} + 1.5 \times \frac{20k}{20k}) = -5.5V$$

5. 圖 5 需用超節點求解

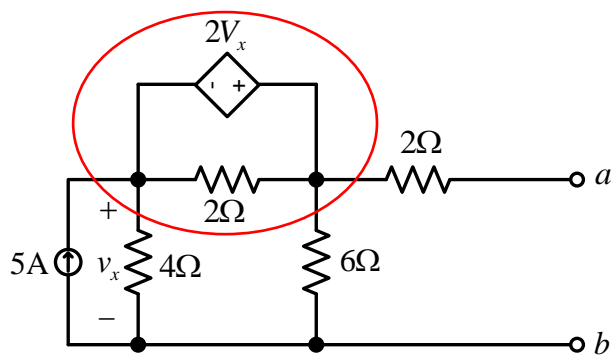
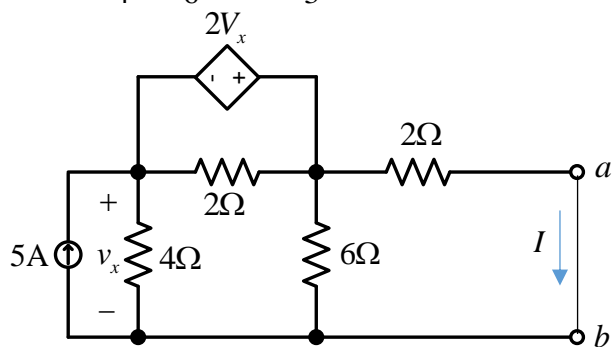
$$5 = \frac{V_x}{4} + \frac{3V_x}{6}, V_x = \frac{20}{3} V, V_{th} = 3V_x = 20V$$




$$\begin{cases} 5 + I = \frac{V_x}{4} - \frac{2V_x}{2} \\ -\frac{2V_x}{2} = I + \frac{3V_x}{6} + \frac{3V_x}{2} \end{cases}$$

$$V_x = \frac{20}{9} V$$


$$I = \frac{10}{3} A = I_{th}$$

$$R_{th} = \frac{V_{th}}{I_{th}} = \frac{20}{\frac{10}{3}} = 6\Omega$$

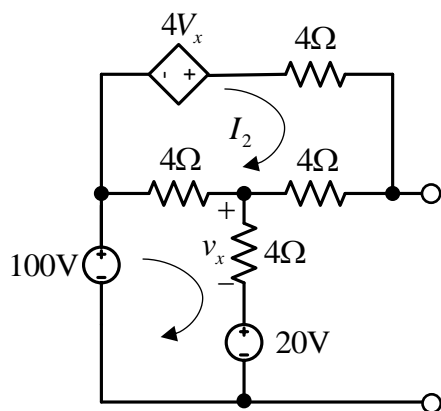6. 圖 6 是一個包含獨立電源與相依電源的戴維寧等效電路, 在此情形下, 將所有電源設為 0 來求得戴維寧等效電阻的方法將不適用, 而須使用開路電壓及短路電流來求等效電阻。


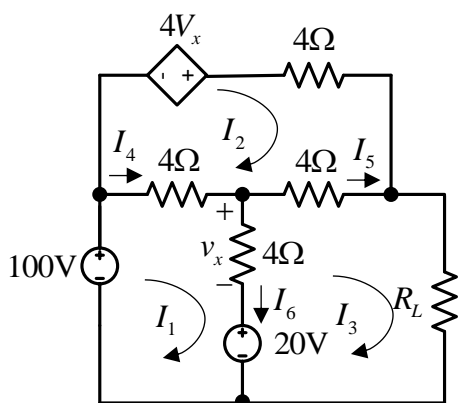
$$\begin{cases} 100 = I_1(4+4) - 4I_2 + 20 \\ 4V_x = I_2(4+4+4) - 4I_1 \\ 20 = -I_1 - 4I_2 + V_{oc} \\ V_x = 4I_1 \\ I_1 = 60\text{A} \\ I_2 = 100\text{A} \\ V_{oc} = 660\text{V} \end{cases}$$



$$\begin{aligned} I_4 &= I_1 - I_2 \\ I_5 &= I_1 - I_3 \\ V_x &= 4I_6 = 4(I_1 - I_3) \\ 100 + 4V_x &= 4I_2 & (6-1) \\ 100 &= 4I_4 + 4I_6 + 20 & (6-2) \\ I_5 &= I_3 - I_2 \\ 4I_1 - 8I_2 + 4I_3 &= 100 & (6-3) \end{aligned}$$

(6-1)~(6-3)式解聯立,

$$\begin{aligned} I_1 &= 60\text{A} \\ I_2 &= 45\text{A} \\ I_3 &= 55\text{A} = I_{oc} \\ R_{th} &= \frac{V_{oc}}{I_{oc}} = 12\Omega \end{aligned}$$

當 $R_L = R_{th}$ 可求得最大功率

$$P_{\max} = \frac{V_{oc}^2}{4R_{th}} = \frac{660^2}{4 \times 12} = 9075\text{W}$$