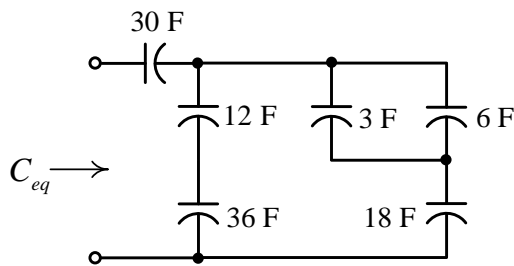
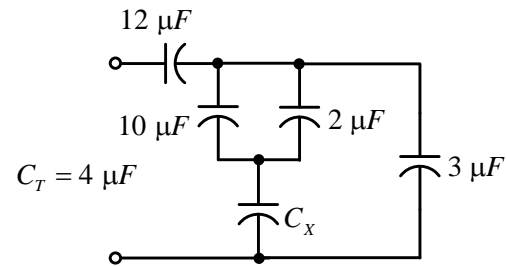


- 1) 滿分 120 分，考試時間 2 小時。
- 2) 答案應有正確之數值與單位。
- 3) 可使用計算器，但不得使用電腦、行動電話等通訊器材。不得參閱任何書本及筆記。
- 4) 請確實遵守考試規則，違反考試規則者，依本校校規處置。

1. Find the value of equivalent capacitance  $C_{eq}$  in the circuit of **Fig. 1**. (10%) **10 F**.
2. Find the value of  $C_X$  in the circuit of **Fig. 2** if the total capacitance  $C_T$  is  $4 \mu\text{F}$ . (15%)  **$4 \mu\text{F}$** .

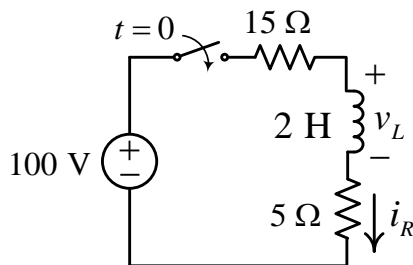


**Fig. 1**

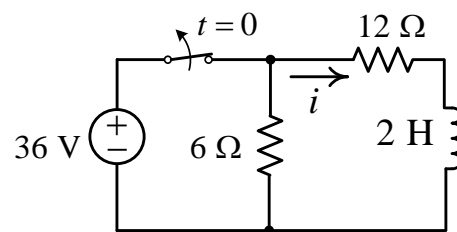


**Fig. 2**

3. The switch in the circuit of **Fig. 3** is closed at  $t=0$ . Find (a) the current  $i_R$ , and (b) the voltage  $v_L$ , for  $t>0$ . (20%) (a)  **$5(1-e^{-10t})$  A**, (b)  **$100e^{-10t}$  V**.
4. In the circuit shown in **Fig. 4**, the switch has been closed for a long time before opening at  $t=0$ . Find the current  $i(t)$  for  $t>0$ . (10%)  **$3e^{-9t}$  A**.

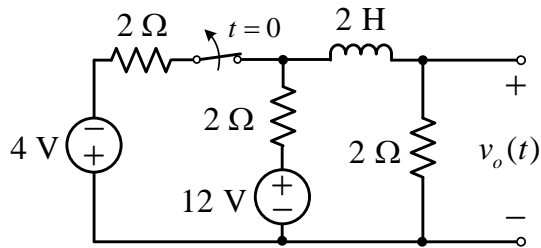


**Fig. 3**

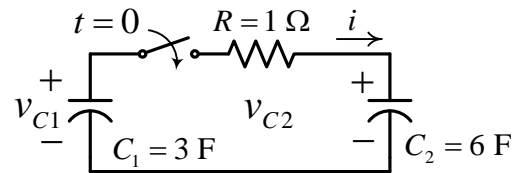


**Fig. 4**

5. The switch in **Fig. 5** has been closed for a long time before opening at  $t=0$ . Find the voltage  $v_o(t)$  for  $t>0$ . (15%)  **$6 - \frac{10}{3}e^{-2t}$  V**.
6. In the circuit of **Fig. 6**, the initial voltages of the capacitors are  $v_{C1}(0^-)=120$  V and  $v_{C2}(0^-)=0$ . The switch closes at  $t=0$ . Find (a) the final values of  $v_{C1}$  and  $v_{C2}$ , (b) the current  $i(t)$  for  $t>0$ , (c) the energy dissipated by the resistor  $R$ . (15%) (Hint: apply the charge conservation principle.)  
(a)  **$v_{C1}=v_{C2}=40$  V**, (b)  **$120e^{-t/2}$  A**, (c) **14400 J**.

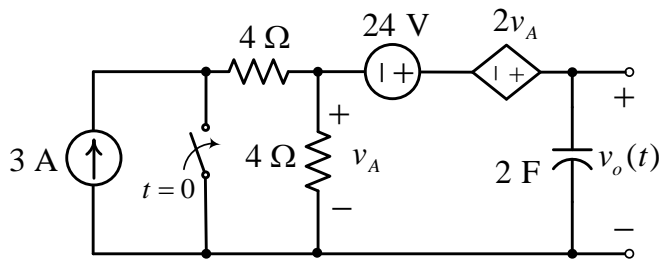


**Fig. 5**

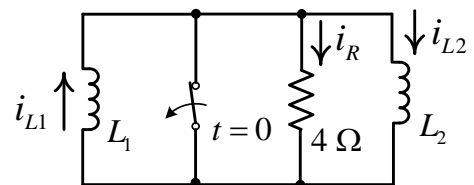


**Fig. 6**

7. The circuit in **Fig. 7** has reached steady-state before the switch closes at  $t=0$ , find  $v_o(t)$  for  $t>0$ . (20%)  $24+36e^{-t/12}$  V.
8. In the circuit shown in **Fig. 8**, inductor  $L_1=6$  H has an initial current of 9 A. The current in inductor  $L_2=12$  H is zero for  $t<0$ . The switch is opened at  $t=0$ . Find (a) the final values of  $i_{L1}$  and  $i_{L2}$ , (b)  $i_R(t)$  for  $t>0$ , (c) the energy dissipated by the 4-Ω resistor. (15%) (Hint, apply the principle of magnetic flux linkage conservation.) (a)  $i_{L1}=i_{L2}=3$  A, (b)  $9e^{-t}$  A, (c) 162 J.



**Fig. 7**



**Fig. 8**